

EECE72545

Power Budget

Matthew Hengeveld

8534331

3/21/2019

Device Power Consumption:

Component/Device	Number of units	Worst case	Standby	Nominal Voltage	Total power	Note
TPS562201	1	750 μ A	1 μ A	14.8V	11 mW	[1]
Power LED	1	0.73 mA	0.73 mA	3V3	2.4 mW	
CAT6219	1	90 μ A	1 μ A	5V	0.45 mW	Quiescent
INA219	1	1 mA	6 μ A	3V3	3.3 mW	
'Heartbeat' LED	1	0.07 mA	0	3V3	231 mW	
ICL3232	1	121 mA	1 μ A	3V3	399 mW	
TX/RX LED	2	2.86 mA	0	3V3	9.5 mW	
MCP2542	1	140 mA	4 μ A	3V3	100 mW	
LCD	1	3 mA	1 mA	5V	15 mW	
LCD Backlight	1	20 mA	0	5V	100 mW	
MCP23S08	1	125 mA	1 μ A	3V3	412.5 mW	
DRV8814	1					[2]
Stepper Motor	1	400 mA	0	14.8V	5.92 W	Half-stepping
DRV8884	1					[3]
DC Motor	2	3 A	0	14.8V	44.4 W	Stall
Fault LED	2	20 mA	0	3V3	66 mW	
74LVC2G14	1	200 mA	8 μ A	3V3	660 mW	Outputs shorted
Servo	1	300 mA	0	5V	1.5W	
HC-10 Bluetooth	1	50 mA	200 μ A	3V3	165 mW	Transmit mode
μ SD Card	1	50 mA	-	3V3	165 mW	Writing
NTC Thermistor	2	2.2 mA	2.2 mA	3V3	7.3 mW	
Ultrasonic Rangefinder	1	20 mA	2.5mA	5V	100 mW	Transmitting

[1] **TPS562201 Power Consumption:**

Worse case power dissipation ($I_{OUT} = 1A$, $25^{\circ}C$):

The following method was taken from TI: Application Report AN-1566 “Techniques for Thermal Analysis of Switching Power Supply Designs”

$$\begin{aligned}
 P_{BIAS} &= I_q \times V_{IN} = 750\mu A \times 14.8V = 0.011W \\
 P_{COND} &= Duty \times [(R_{DS(ON)HS} \times I_{OUT}^2) + (R_{DS(ON)LS} \times I_{OUT}^2)] \\
 &= 35\% \times [(0.14\Omega \times 1A^2) + (0.084\Omega \times 1A^2)] \\
 &= 0.078W \\
 P_{SW} &= \frac{(I_{OUT} \times V_{IN})}{2} \times f_{SW} \times (t_R + t_F) \\
 &= \frac{(1A \times 14.8V)}{2} \times 580KHz \times (50ns) = 0.215W \\
 P_{TOTAL} &= P_{BIAS} + P_{COND} + P_{SW} = \mathbf{0.31W}
 \end{aligned}$$

^[2] **DRV8814 Power Consumption:**

The DRV8814 has internal 5V and 3V3 regulators.

Worse case power dissipation ($V_M = 14.8V$, $I_{OUT} = 1.5A$, $25^\circ C$):

$$\begin{aligned}
 P_{RDS(ON)} &= (2)(R_{DS(ON)HS+LS})(I_{OUT}^2) = (2)(0.525\Omega)(1.5A^2) = 2.36W \\
 P_{SW} &= (V_M)(I_{OUT})(t_{F,R})(f_{SW}) = (14.8V)(1.5A)(300ns)(50KHz) = 0.333W \\
 P_{IVM} &= (V_M)(I_{IVM}) = (14.8V)(5mA) = 0.074W \\
 P_{LDO} &= (V_M - V_{LDO})(I_{LDO OUT}) = (14.4V - 3.3V)(1mA) = 0.0115W \\
 P_{TOTAL} &= P_{RDS(ON)} + P_{SW} + P_{IVM} + P_{LDO} = \mathbf{2.775W}
 \end{aligned}$$

^[3] **DRV8884 Power Consumption:**

The DRV8884 has internal 5V and 3V3 regulators.

Worse case power dissipation ($V_M = 14.8V$, $I_{OUT} = 0.4A$, $25^\circ C$):

$$\begin{aligned}
 P_{RDS(ON)} &= (R_{DS(ON)HS})(I_{OUT}^2) + (R_{DS(ON)LS})(I_{OUT}^2) \\
 &= (0.798\Omega)(0.4A^2) + (0.749\Omega)(0.4A^2) = 0.247W \\
 P_{SW} &= (V_M)(I_{OUT})(t_{F,R})(f_{SW}) = (14.8V)(0.4A)(100ns)(50KHz) = 0.029W
 \end{aligned}$$

$$P_{IVM} = (V_M)(I_{IVM}) = (14.8V)(5mA) = 0.074W$$

$$P_{TOTAL} = P_{RDS(ON)} + P_{SW} + P_{IVM} = \mathbf{0.35W}$$

Per Rail Power Consumption:

Rail	Total Power
5V	1715.45 mW
3V3	2311 mW

Efficiency Corrected Power Consumption:

Because the 5V and 3V3 rails are converted from the battery voltage, there are losses associated with each conversion. The efficiency of the TPS562201 is about 91% at 300mA, and the CAT6219, being a linear regulator, is about 50%. Therefore, 3V3 rail could draw a total 2.888W from the 5V rail. The 5V rail, along with the previously calculated 3V3 draw, could draw a total 5.058W from the 14.8V battery.